

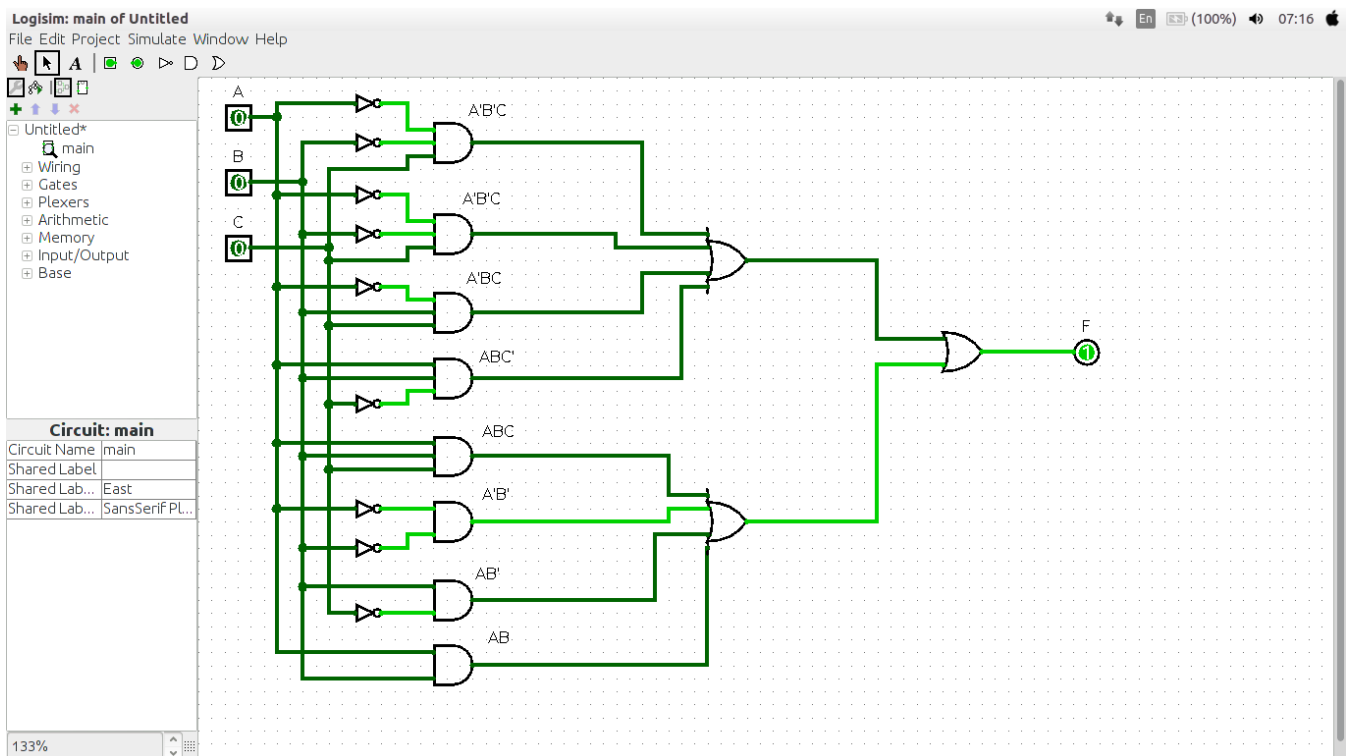
 


Lab : 1

$$F1 = A'B'C + A'B'C + A'BC + ABC' + ABC + A'B' + BC' + AB$$

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

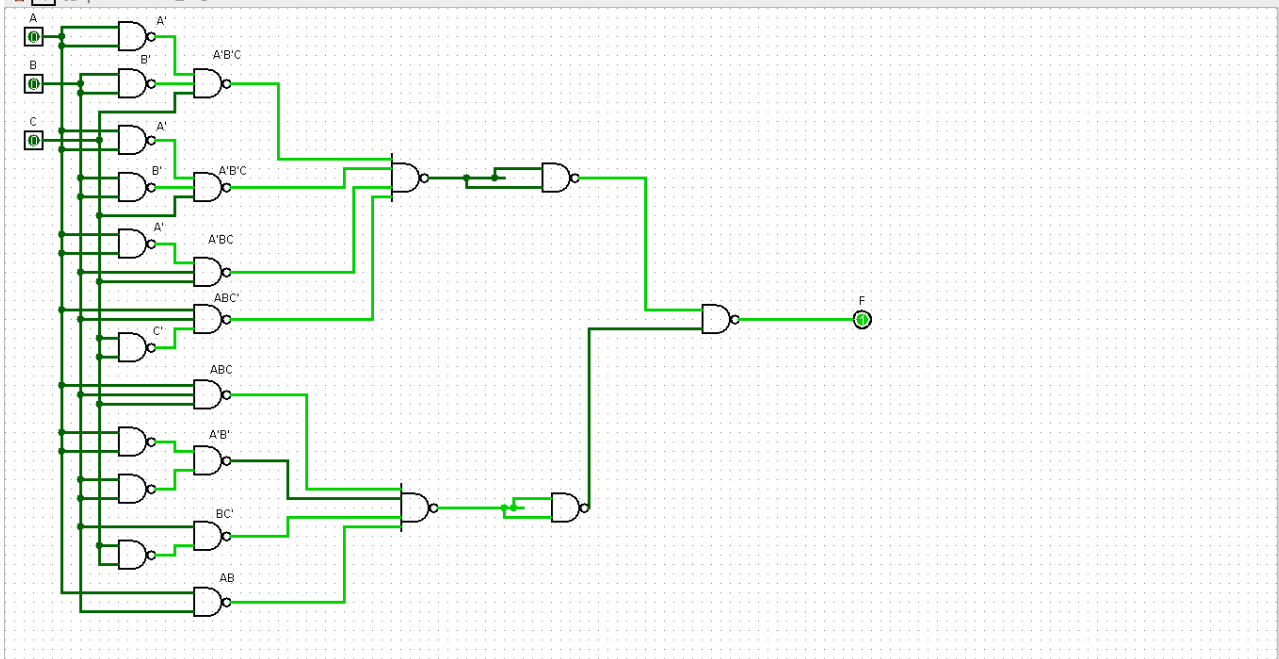

 

Untitled 4*


- main
- Wiring
- Gates

- NOT Gate
- Buffer
- AND Gate
- OR Gate
- NAND Gate
- NOR Gate
- XOR Gate
- XNOR Gate
- Odd Parity
- Even Parity
- Controlled Buffer

Circuit: main



Circuit Name	main
Shared Label	
Shared Label...	East
Shared Label...	SansSerif Pla...


100%

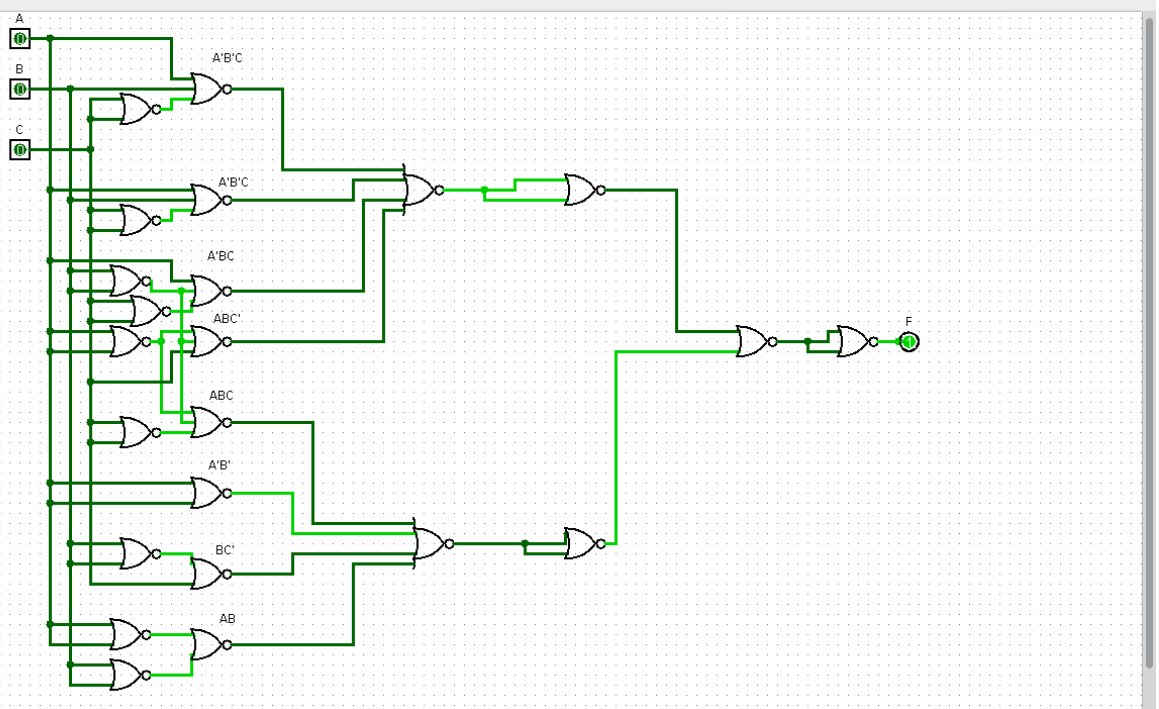

$F2 = A'B'C'D + AB'C'D + A'BC'D + ABC'D + A'BCD + ABCD$

A	B	C	D	F2
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

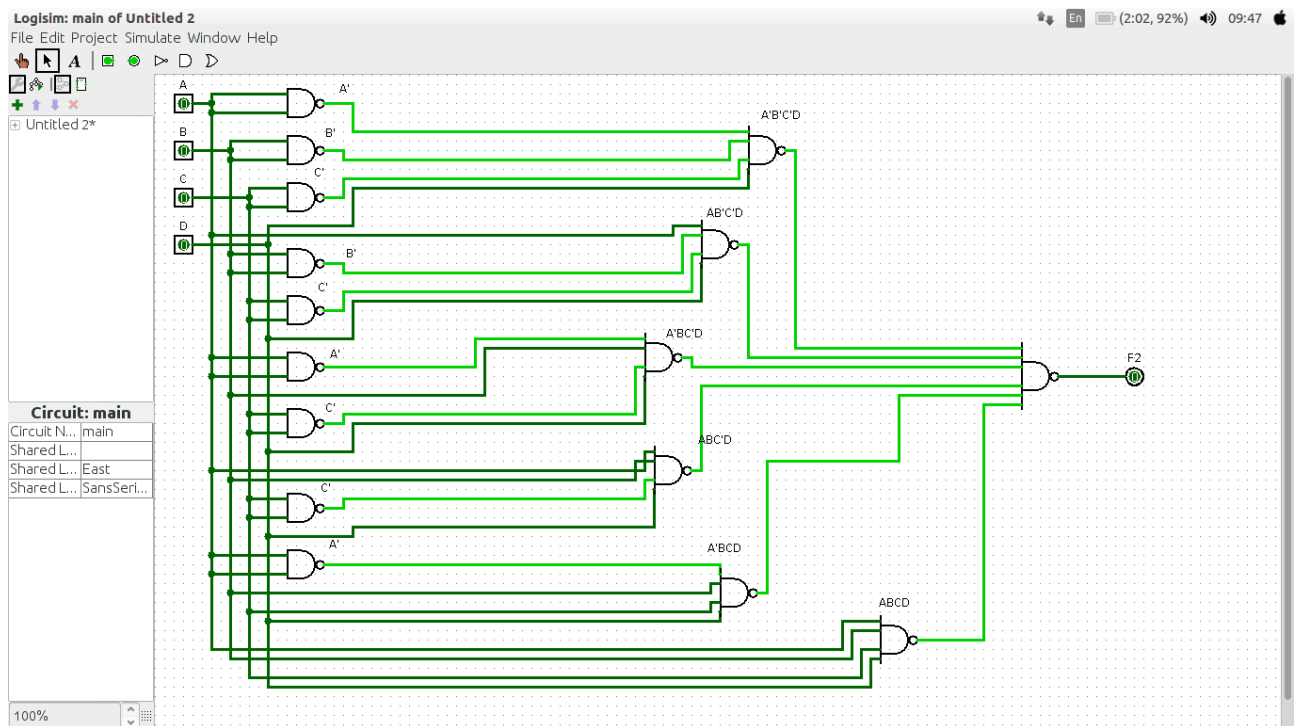
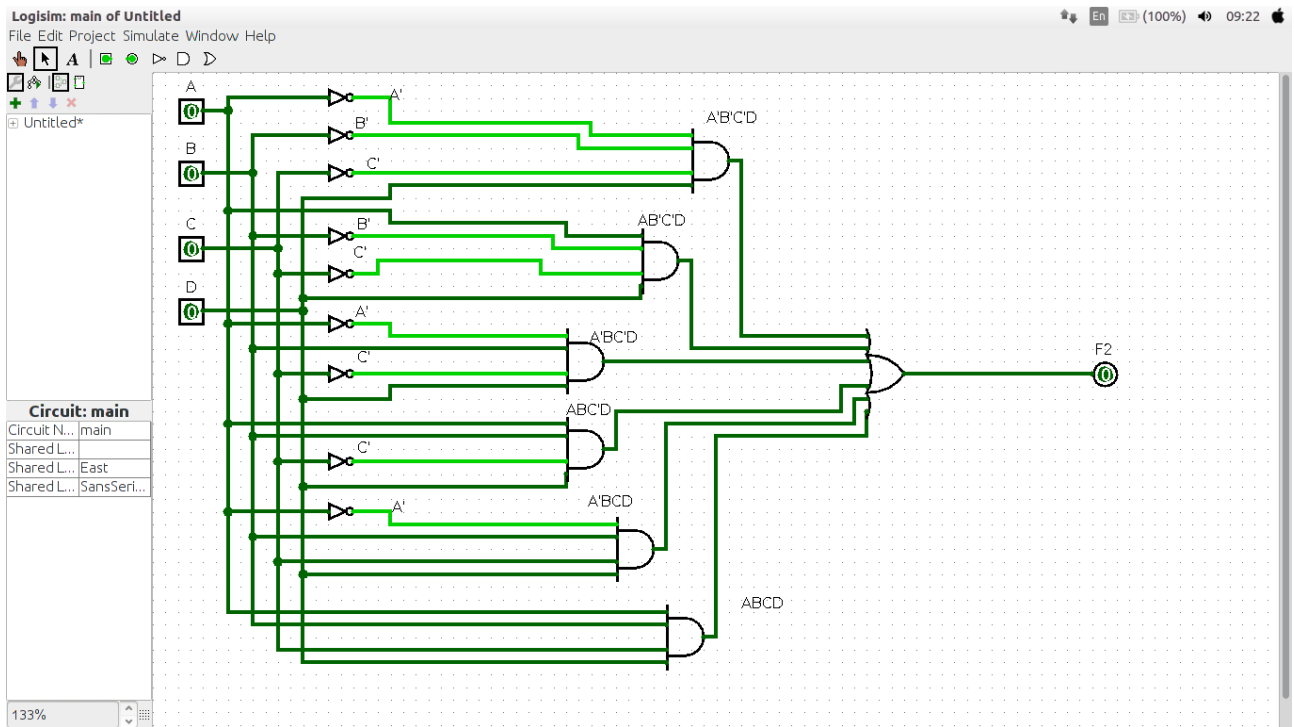


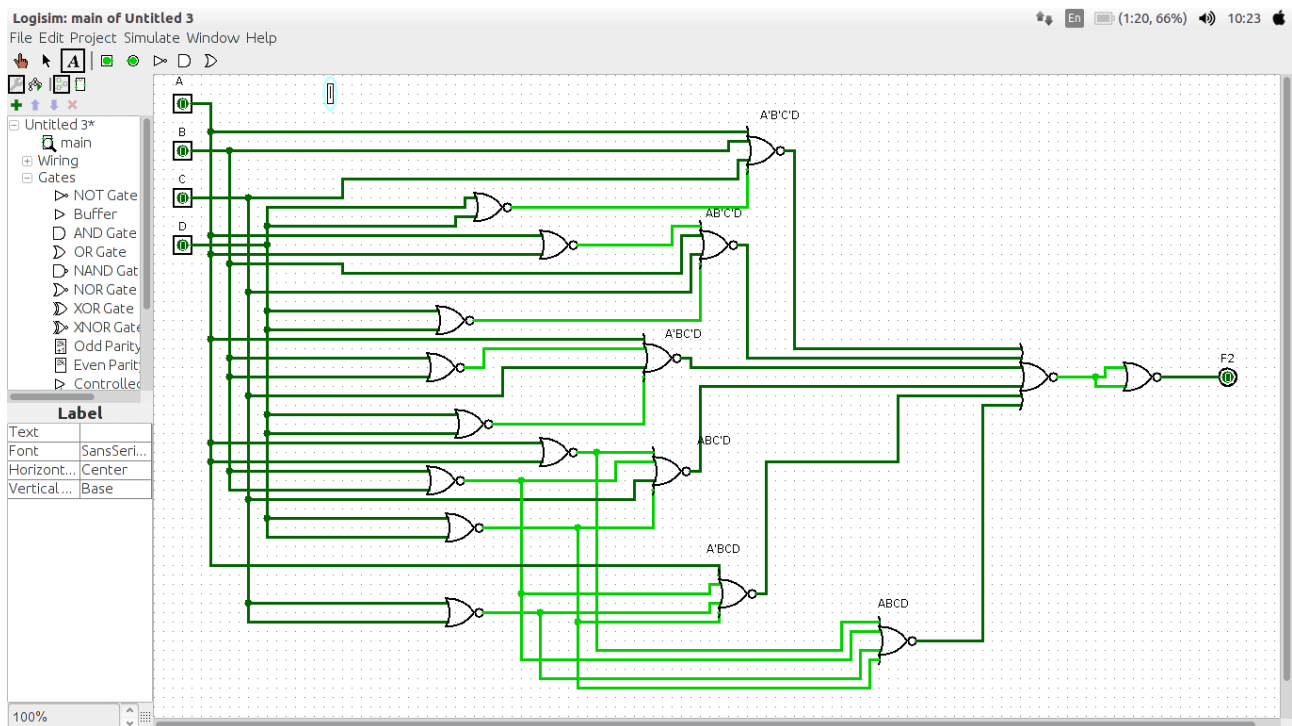


$$F3 = AB + A'BC'D + A'BCD + AB'C'D$$

A	B	C	D	F3
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1



1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

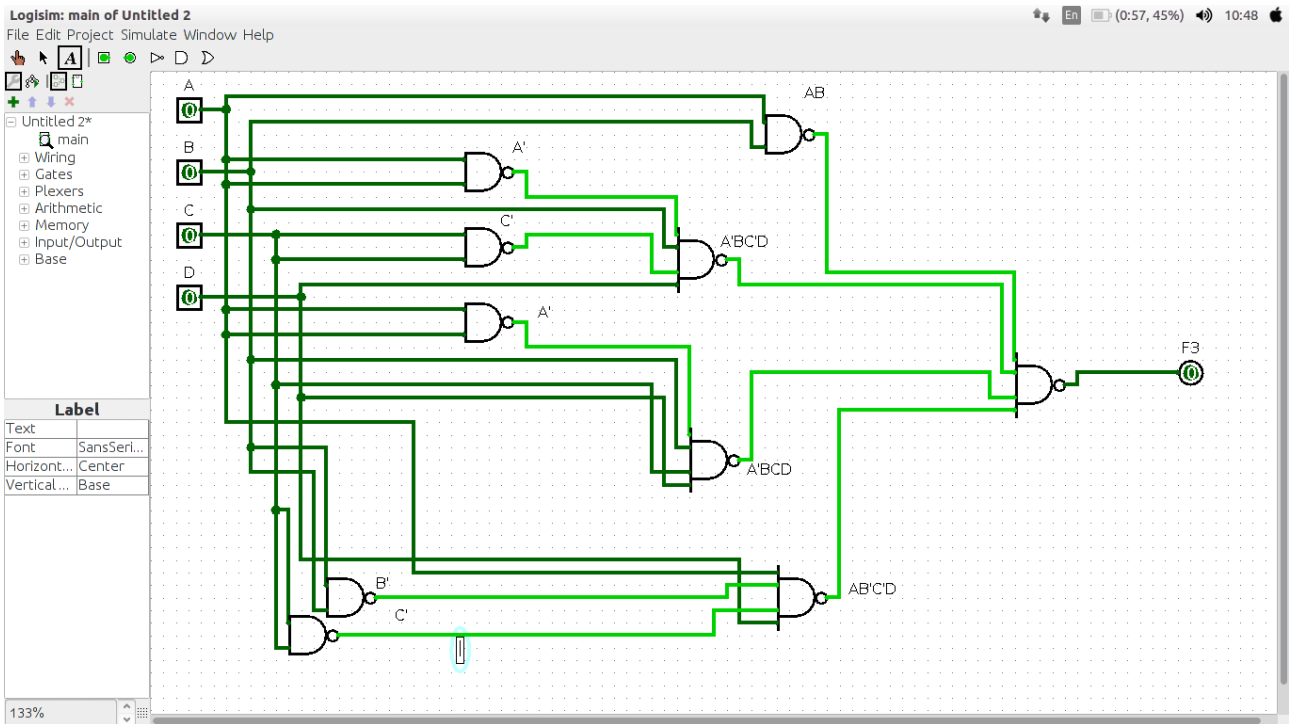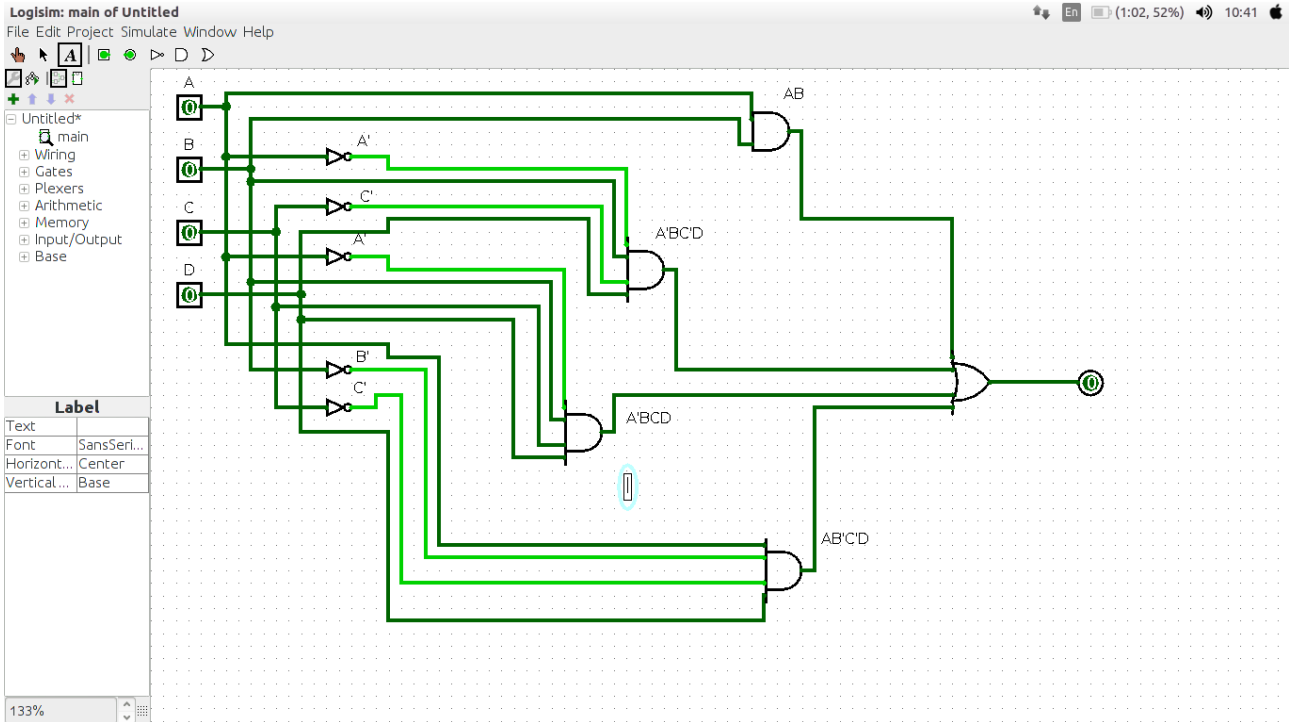


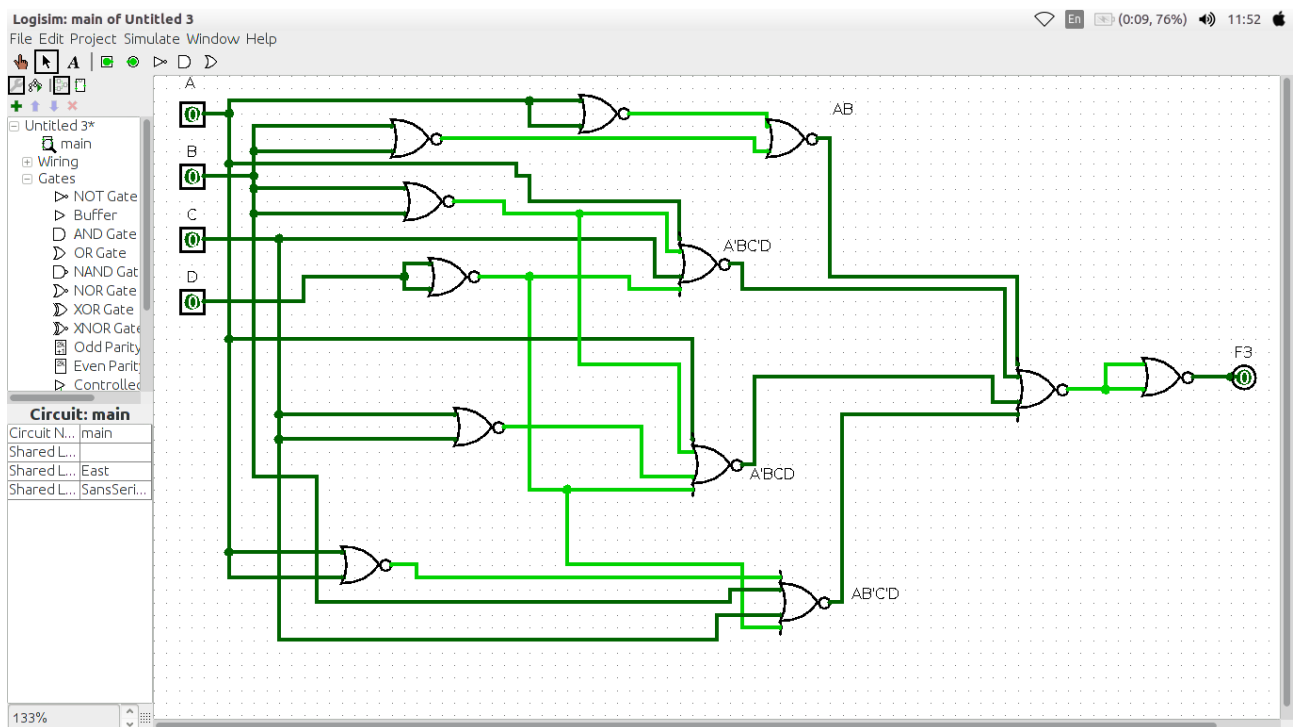

$F4 = C + S$ where $C = xy + xz + yz$ and $S = C' (x + y + z) + xyz$

x	y	z	F4
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

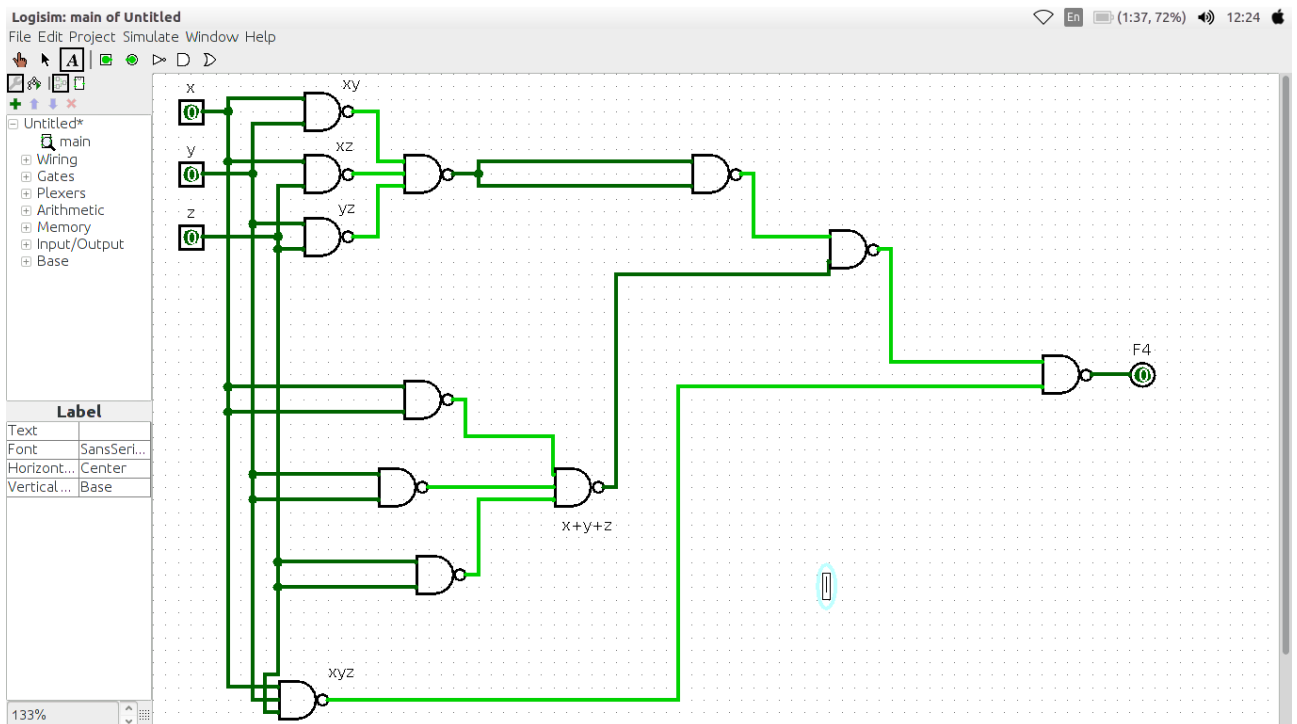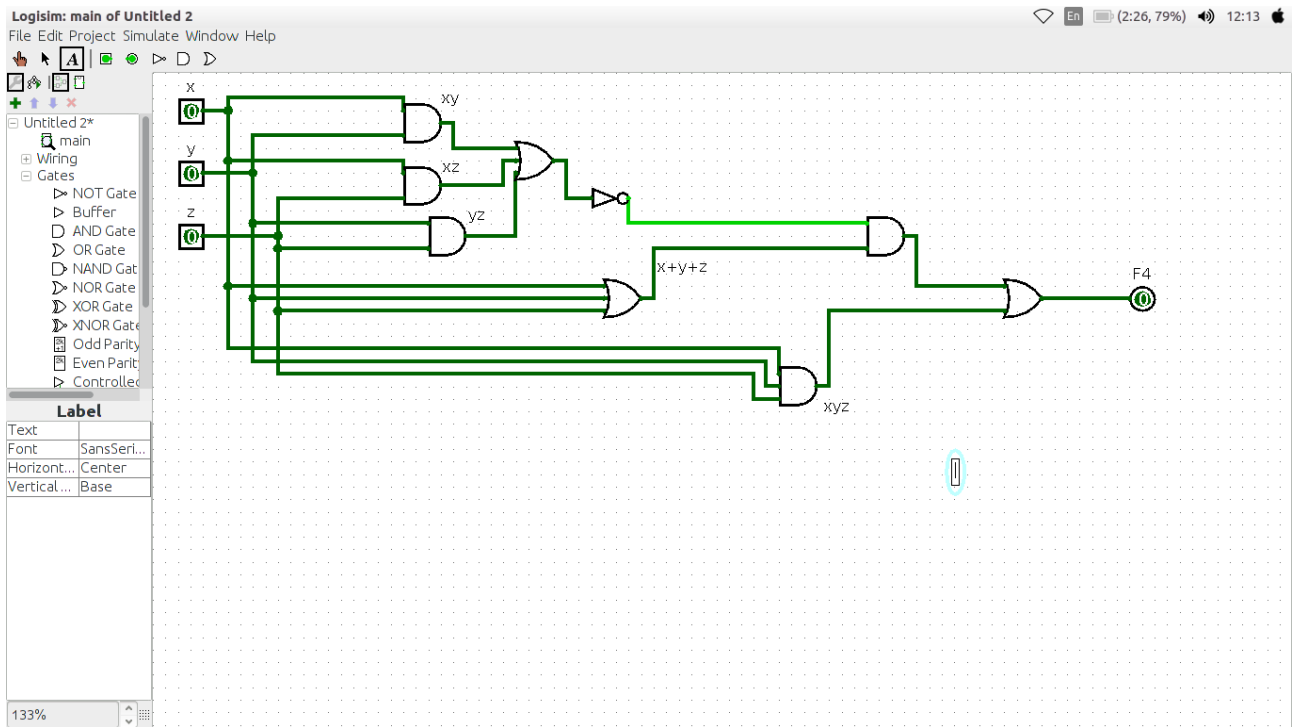

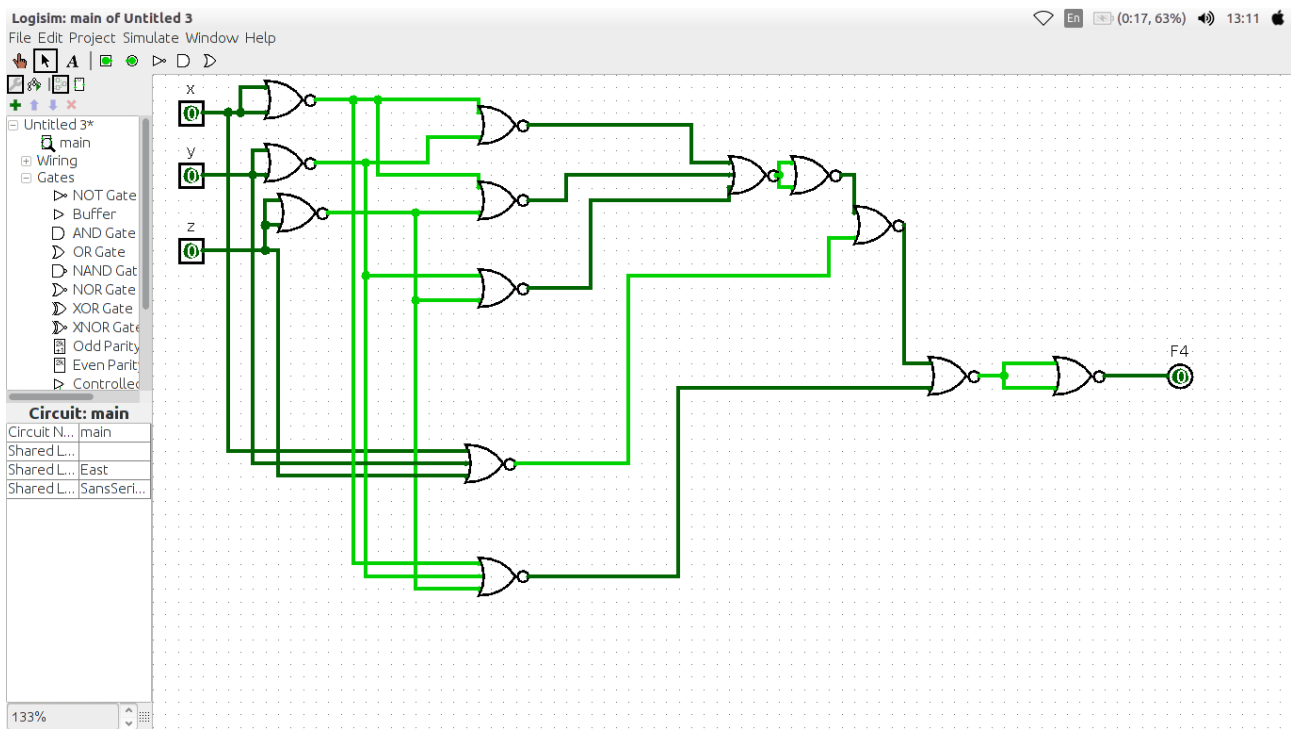

Lab: 2-3

$$F1 = A'B' + AB'C + 'BC + AB' + C + AB' + C' + AB$$

1.


A	B	C	F1
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1


2.

Min terms = $A'B'C' + A'B'C + A'BC' + A'BC' + AB'C + AB'C' + ABC' + ABC$


Max terms = no Max terms

3.

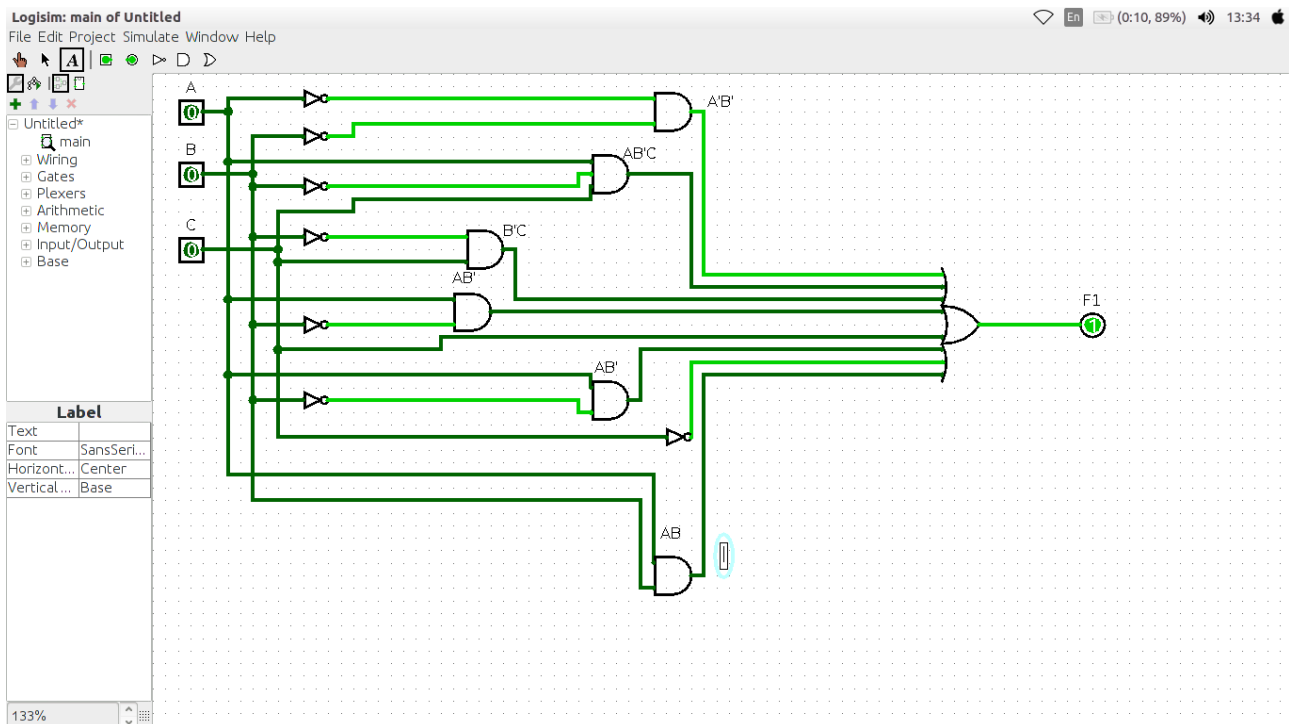

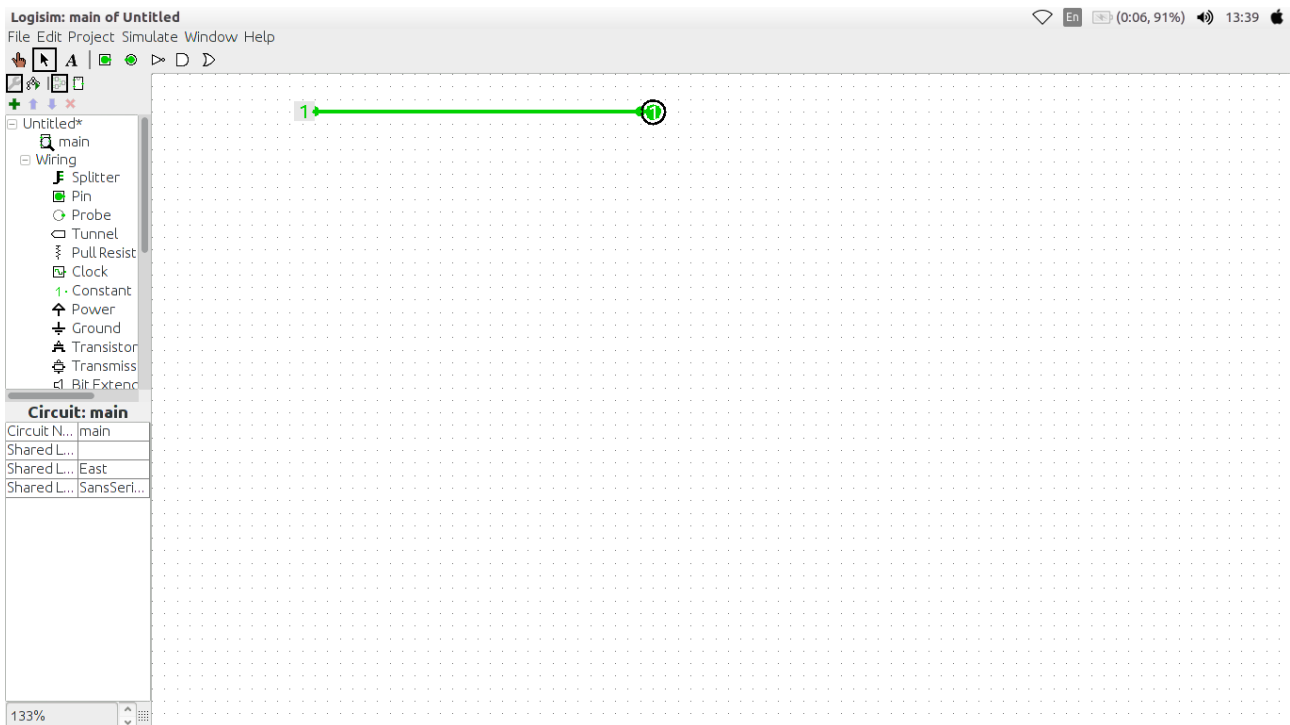

4.

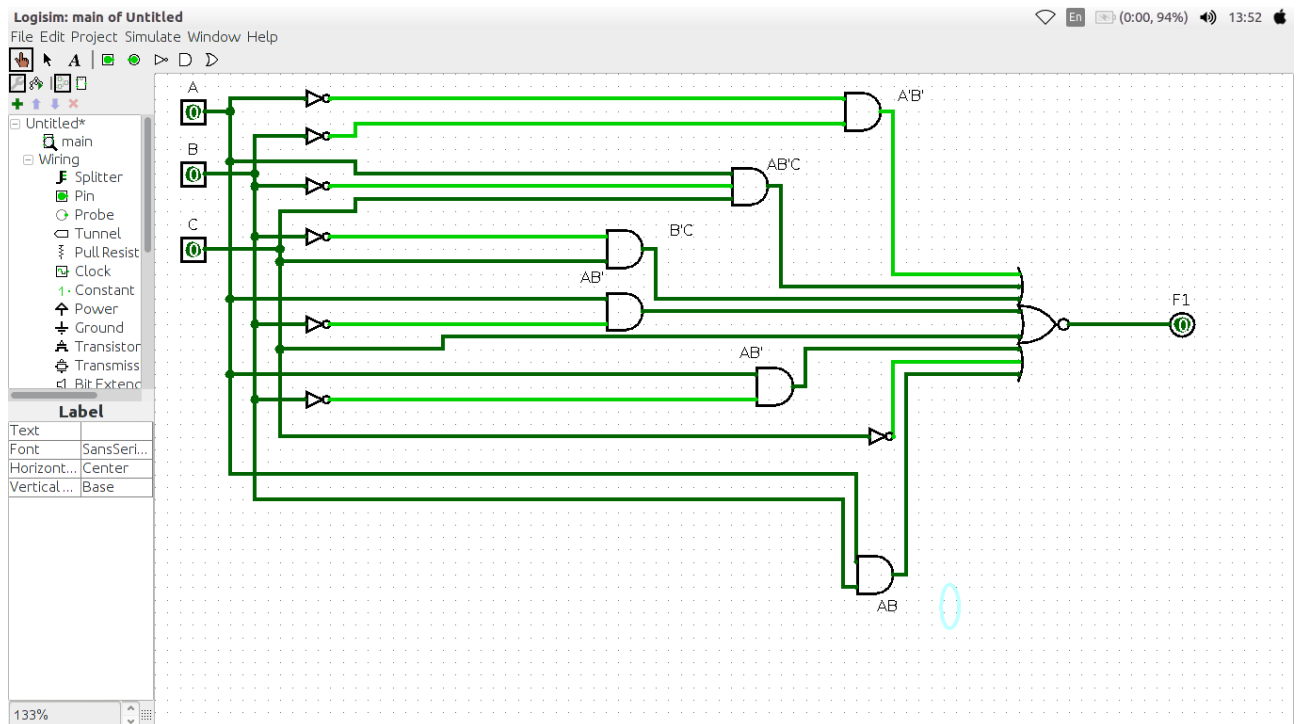

$$F2 = AB'C'D + ABC'D + BC'D + A'B + AD$$

1.


A	B	C	D	F2
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1


2.

Min Terms = $A'B'C'D + A'BC'D' + A'BC'D + A'BCD' + A'BCD + AB'C'D + AB'CD + ABC'D' + ABC'D + ABCD$


MaX Terms = $(A+B+C+D)(A+B+C'+D)(A+B+C'+D')(A'+B+C+D)(A'+B+C'+D)(A'+B'+C'+D)$

3.

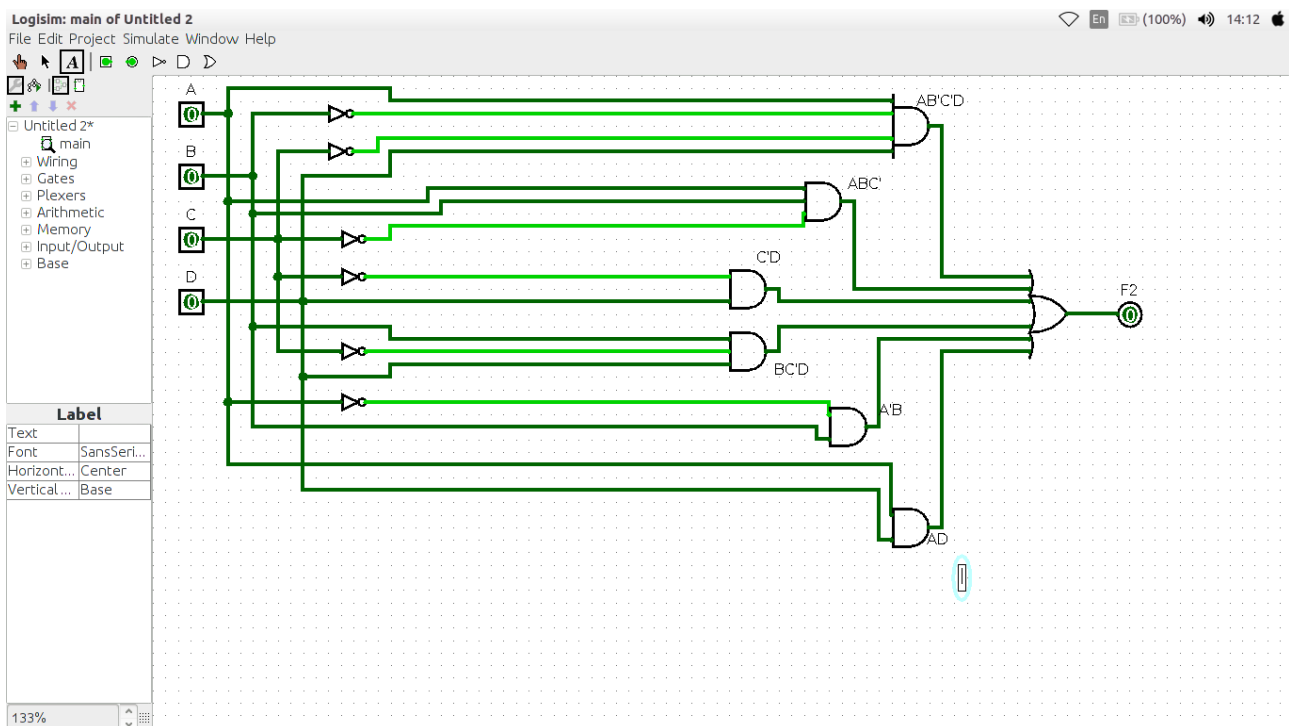

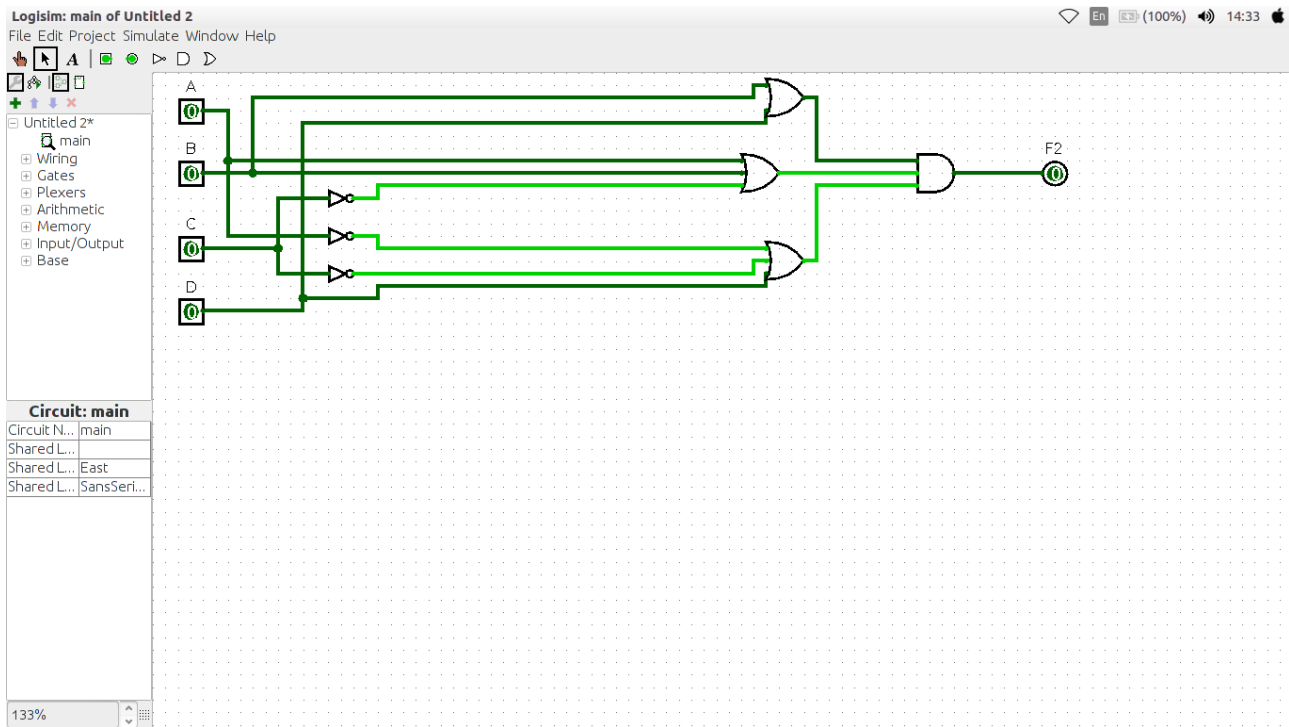

4.

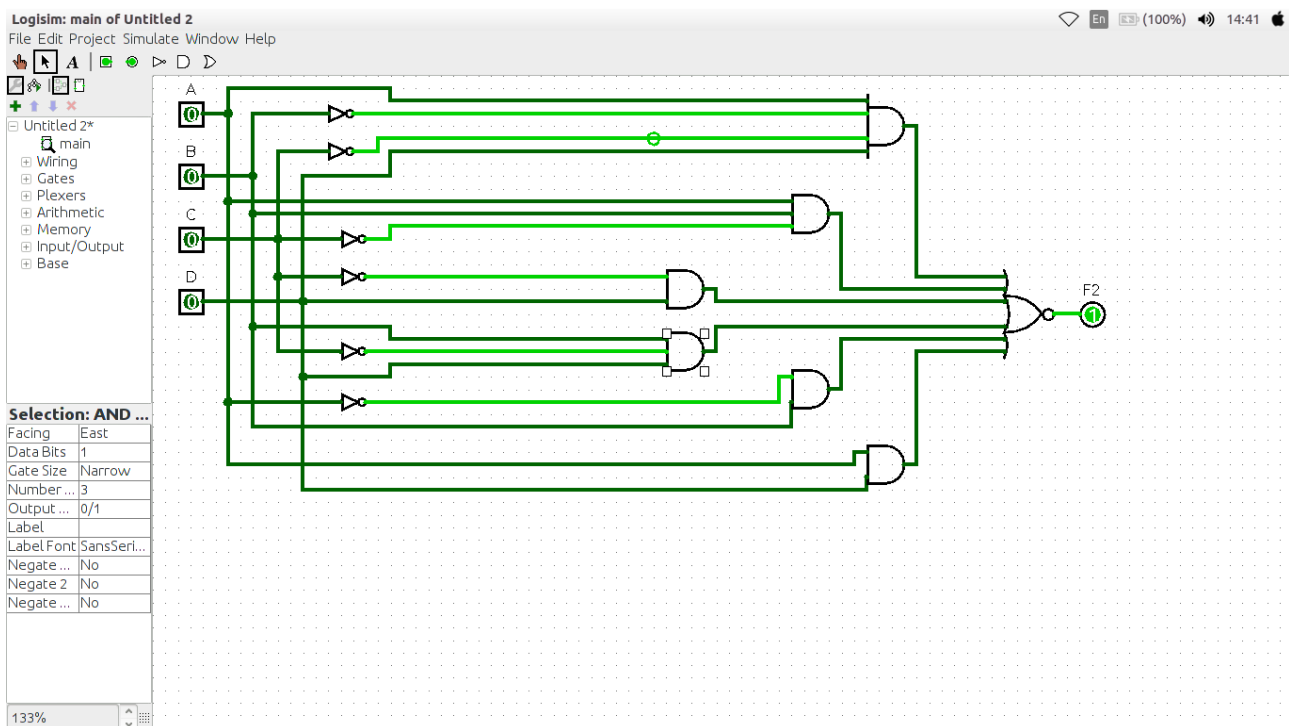

$$F3 = AB + A'B'D + A'B + AB'C'D$$

1.

A	B	C	D	F3
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

2.

Min Terms = $A'B'C'D + A'B'CD + A'BC'D' + A'BC'D + A'BCD'$
 $A'BCD + AB'C'D + ABC'D' + ABC'D + ABCD' + ABCD$

Max Terms = $(A+B+C+D)(A+B+C'+D)(A'+B+C+D)$
 $(A'+B+C'+D)(A'+B+C'+D')$

3.

Logisim: main of Untitled 2

File Edit Project Simulate Window Help

⏏ 🔍 A | 🟢 🟡 ⚙️ ▶️ ⏏️ ⏏️




- Untitled 2*
- main
- Wiring
- Gates
- Plexers
- Arithmetic
- Memory
- Input/Output
- Base

Selection: AND ...

Facing	East
Data Bits	1
Gate Size	Narrow
Number ...	2
Output ...	0/1
Label	
Label Font	SansSerif
Negate ...	No
Negate ...	No

133%

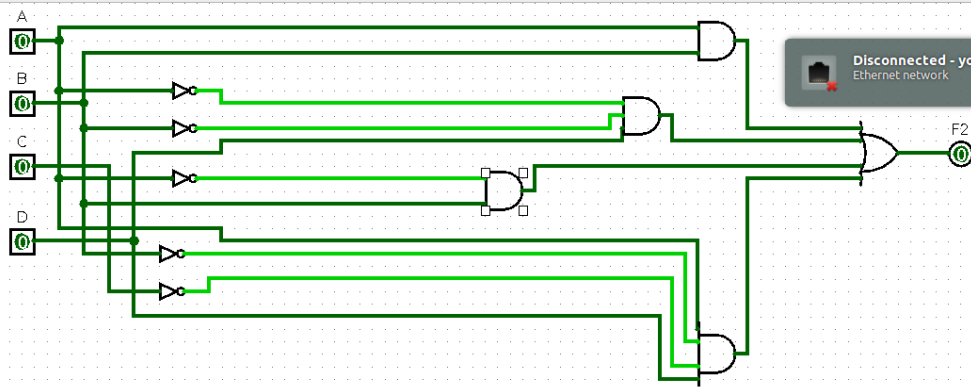

Logisim: main of Untitled 2

File Edit Project Simulate Window Help

⏏ 🔍 A | 🟢 🟡 ⚙️ ▶️ ⏏️ ⏏️




- Untitled 2*
- main
- Wiring
- Gates
- Plexers
- Arithmetic
- Memory
- Input/Output
- Base


Selection: OR G...

Facing	East
Data Bits	1
Gate Size	Narrow
Number ...	3
Output ...	0/1
Label	
Label Font	SansSerif
Negate ...	No
Negate 2	No
Negate ...	No

133%

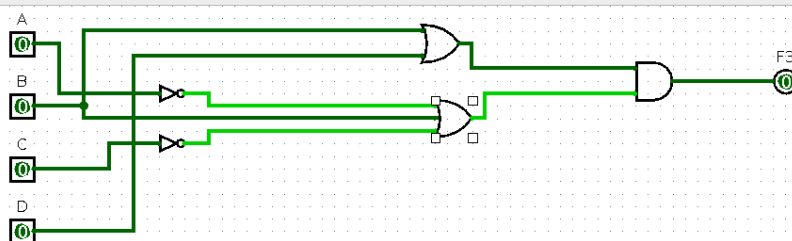

4.

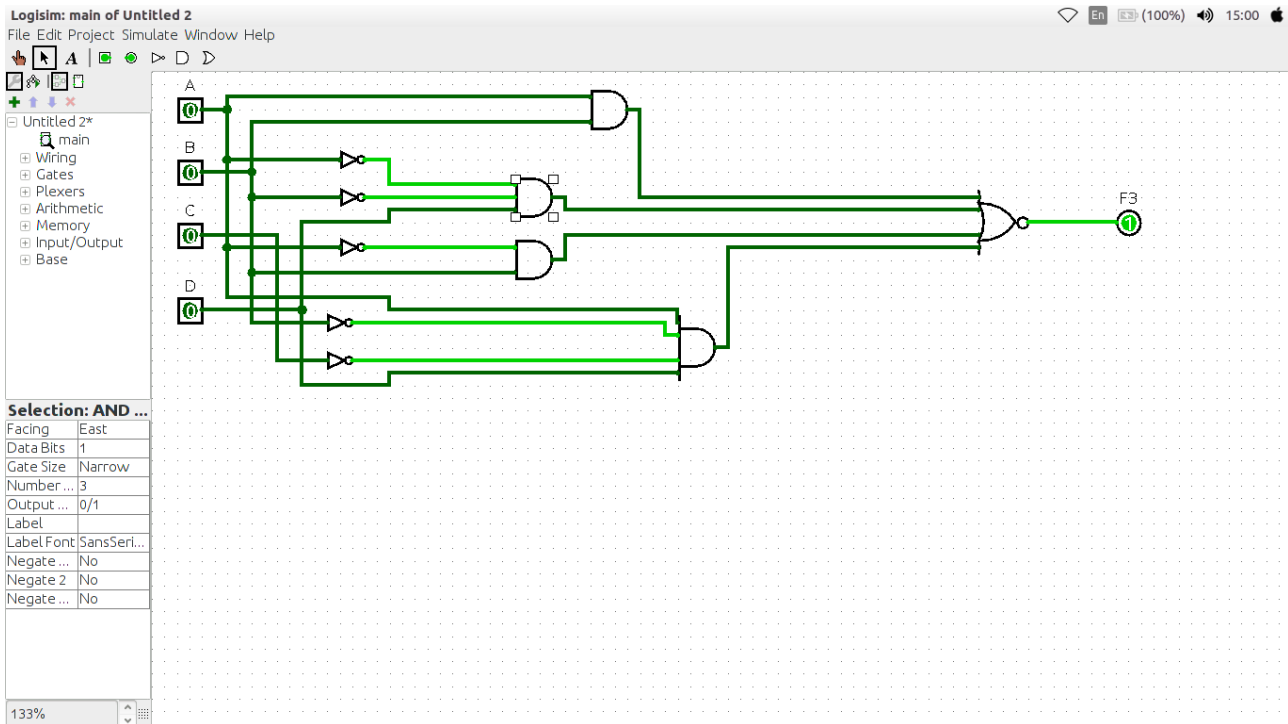

$$F4 = C + S \text{ where } C = xy + yz \text{ and } S = C' (x + y) + xyz$$


x	y	z	F4
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

2.

Min Terms = $x'yz' + x'yz + xy'z' + xy'z + xyz' + xyz$

Max Terms = $(x+y+z)(x+y+z')$

3.

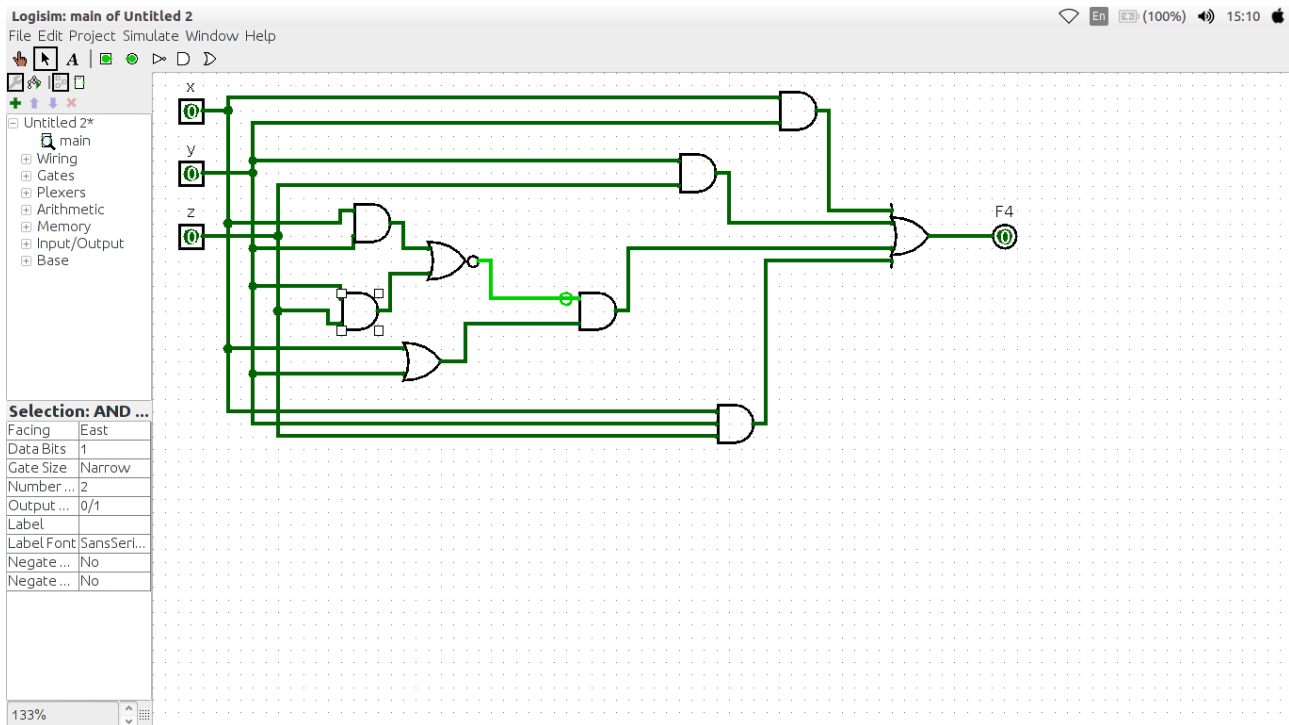

Lab: 4-5

$$F1 = A'B' + AB'C + A'BC + AB' + C + AB' + C' + AB$$

1.

A	B	C	F1
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1


2.

K-MAP

1	1	1	1
1	1	1	1

EQUATION IS : 1

3.

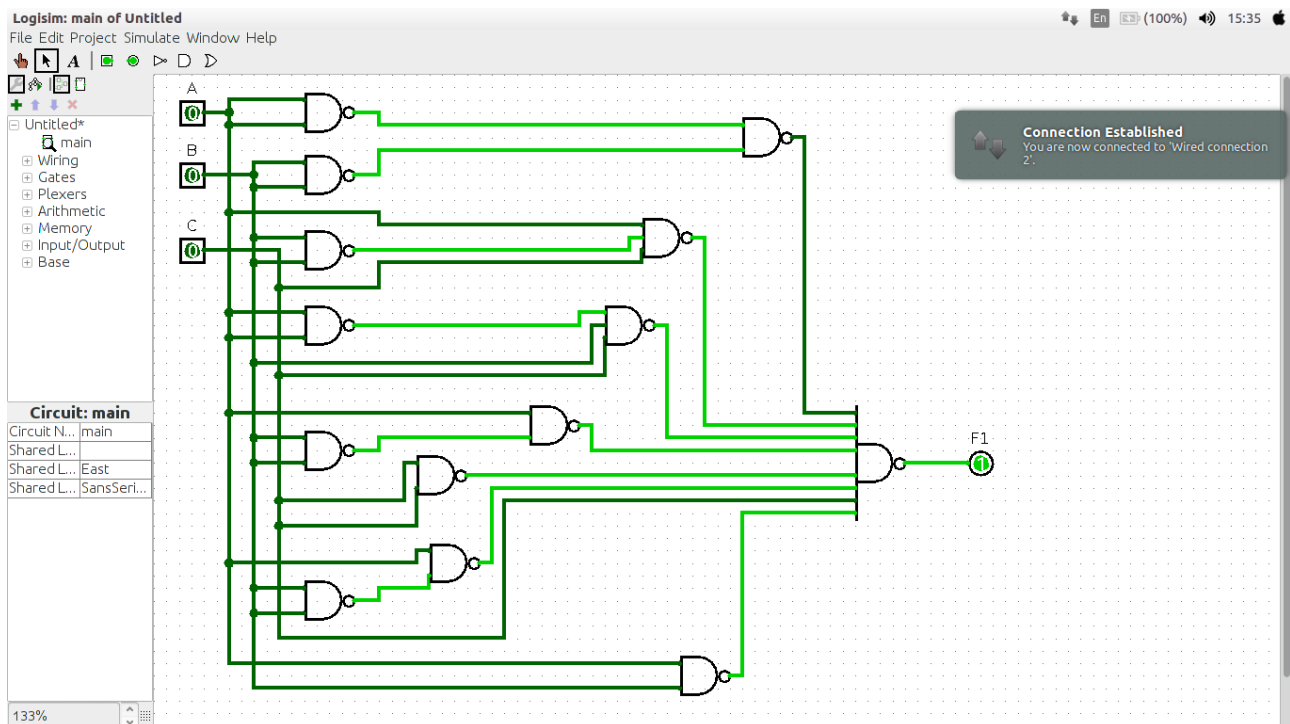

$$F2 = AB'C'D + AC'D + C'D + C'D + A'B + AD$$

1.

A	B	C	D	F2
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1

1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1


2.

K-MAP

0	1	0	0
1	1	1	1
0	1	1	0
0	1	1	0

EQUATION IS : $C'D + A'B + AD$

3.

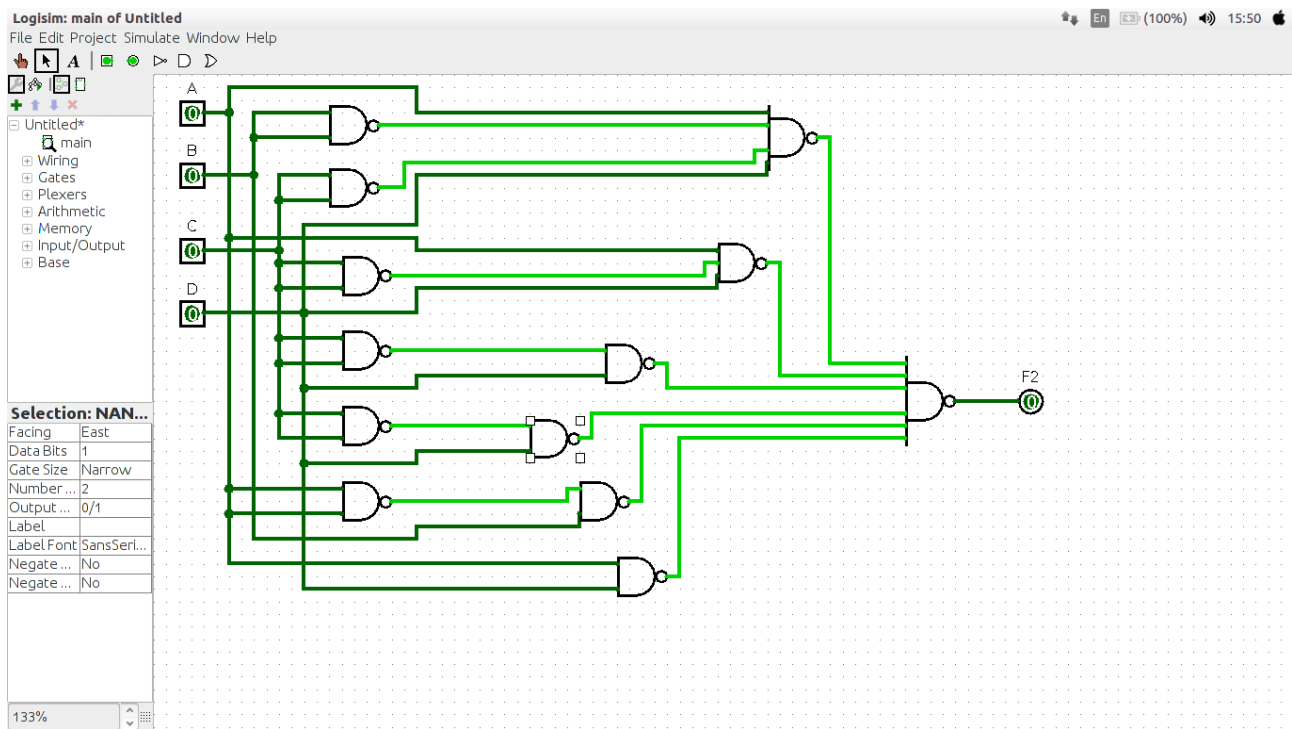

$$F3 = AB + A'C'D + A'BD + AB'C'$$

1.

A	B	C	D	F3
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0

1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1


2.

K-MAP

0	1	0	0
0	1	1	0
1	1	1	1
1	1	0	0

EQUATION IS : $C'D + BD + AC' + AB$

3.

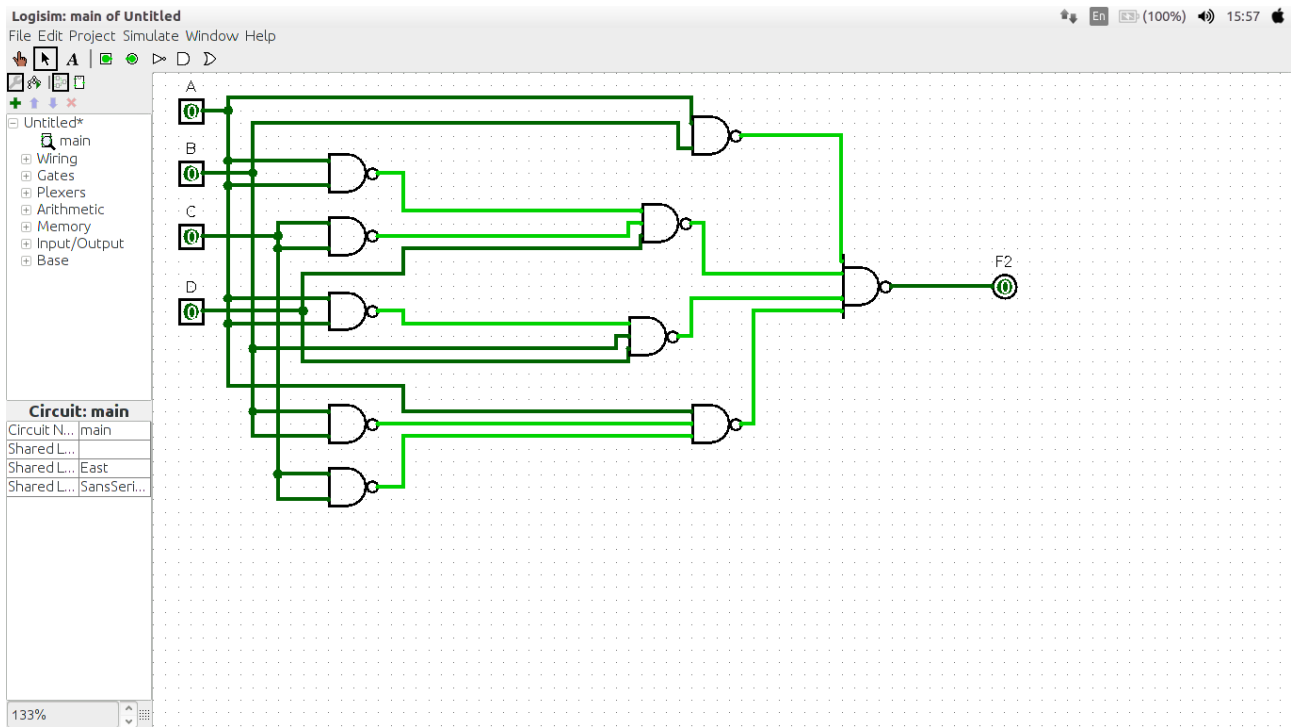

$F4 = C + S$ where $C = xy + yz$ and $S = C' (x + y) + xyz$

1.

x	y	z	F4
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

2.

k-map

0	0	1	1
1	1	1	1

Equation is : $x + y$

3.

